

Cell	Battery	Switch	Lamp	Ammeter	Volt meter	Diode	LED	LDR	Fuse	Resistor	Variable resistor	Thermistor	Motor
Store of chemical energy	Two or more cells in series	Breaks circuit, turning current off	Lights when current flows	Measures current	Measures potential difference	Current flows one way	Emits light when current flows	Resistance low in bright light	Melts when current is too high	Affects the size of current flowing	Allows current to be varied	Resistance low at high temp	Converts electrical energy into mechanical energy



# EDEXCEL TOPIC 10 ELECTRICITY AND CIRCUITS

## Current, Potential difference, Charge and Energy.

## Atom structure

Particle	Charge	Size	Found
Proton	+	1	In the nucleus
Neutron	None	1	
Electron	-	Tiny	Orbits the nucleus

Series	A circuit with one loop
Parallel	A circuit with two or more loops

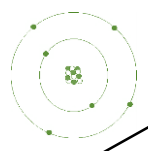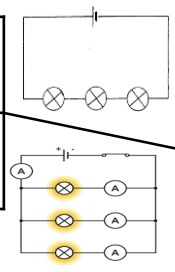

Ammeter	Set up in series with components	Measures current in amps in the component
Volt meter	Set up parallel to components	Measures p.d. in volts across the component

Potential difference	The energy transferred by a component for every per unit of charge passed	1 volt = 1 joule per coulomb (1V = 1J/C)
----------------------	---	--

$E = Q \times V$  Energy transferred = Charge moved X potential difference

$Q = I \times t$  Charge = Current X time

Current is conserved at a junction in a circuit.

$V = I \times R$  Potential difference = Current X Resistance

Resistance	Series circuit	Parallel circuit
	Ammeter readings are the same.	Ammeter readings are shared between branches.
	Volt meter readings are shared.	Volt meter readings are the same.
	Total resistance increases as you add resistors in series.	Total resistance decreases as you add resistors in parallel.

Resistance Ohms ( $\Omega$ ) **A measurement of how much current flow is reduced**

The higher the resistance, the more difficult it is for current to flow.

Increasing resistance, reduces current.

Increasing voltage, increases current.


Current	Flow of electrical charge	Ampere (A)
Potential difference (p.d.)	How much electrical work is done by a cell	Volt (V)
Charge	Amount of electricity travelling in a circuit	Coulomb (C)

Current in metals is the flow of electrons.

Current only flows when the circuit is closed and there is a p.d. across a component.

### Core Practical

Relationship between p.d., current and resistance of a lamp and resistor	To test series and parallel circuits using resistors and lamps
Circuit set up like standard test circuit.	

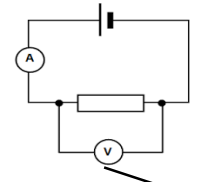

Standard test circuit **Used to investigate relationship between current, p.d. and resistance of components**


Insert variable resistor, in series, to change current and measure current and p.d.

Energy transferred	Joules (J)
Charge	Coulombs (C)
Potential difference	Volts (V)
Current	Amps (A)
Time	Seconds (s)
Resistance	Ohms ( $\Omega$ )



Thermistor	LDR
Resistance varies with temperature	Resistance varies with light intensity
Resistance decreases as temperature increases.	Resistance decreases as light increases.

Fixed resistor	At a constant temperature, current is directly proportional to the p.d. across the resistor.
Filament lamp	As current increases, the resistance increases. The temperature increases as current flows.
Diode	Current flows when p.d. flows forward. Very high resistance in reverse.

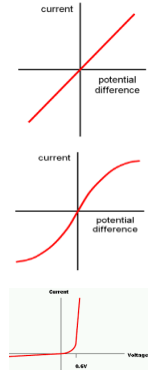

# EDEXCEL TOPIC 10 ELECTRICITY AND CIRCUITS

3 pin plug	<b>Live - Brown</b>	Carries p.d from mains supply.	p.d between live and earth = 230V
	<b>Neutral - Blue</b>	Completes the circuit.	p.d. = 0V
	<b>Earth - Green and Yellow stripes</b>	Only carries current if there is a fault.	p.d. = 0V

**HIGHER ONLY**

Reducing unwanted energy transfer  
Use low resistance metals in wire. Thicker wires have lower resistance. Resistance can be decreased by cooling wires so the lattice ions do not vibrate as much.

Energy transfer  
**Electrons flow through lattice of vibrating ions, they collide with ions.**  
The more collisions, the harder it is for electrons to pass through so higher electrical resistance.

$P = E \div t$   
Power = Energy transferred ÷ time

Safety features	<b>Fuse</b>	Thin wire inside the plug connected to live wire.	If current exceeds a certain value, the wire melts breaking the circuit.
	<b>Circuit breaker</b>	'Trips' the switch.	Detect change in current and switch off the supply.
	<b>Switch</b>	Connected to the live wire.	When turned off, no current goes through the appliance.
	<b>Earthing</b>	Earth wire joins the metal case.	Earth wire takes current to the ground instead of conducting in the metal.

## Electrical safety

Electric shock  
**A connection between the live wire and earth**  
The live wire carries 230V, your body is at 0V so there is a large potential difference across your body and current flows through you.

Power rating  
**Power rating measured in watts**  
The power rating equals the number of joules transferred every second by the device from mans electrical supply to an energy store.

Power  
**Energy transferred per second**  
Measured in Watts (W).

Power transfer  
**Depends on p.d. across and current flowing through device**  
Both affect the rate of energy transfer and the rate at which energy is transferred to other energy stores.  
Current equals how much charge passes per unit time.  
p.d. equals how much energy each unit of charge transfers.

Power (W) = current X potential difference  $P = I \times V$   
Power = (current)<sup>2</sup> X resistance  $P = I^2 \times R$

## Transferring energy


Thermal energy dissipates into surroundings thermal energy store and the temperature rises.

Energy transferred by heating and the resistor becomes warmer.

Current in a resistor  
**When current flows circuits warm up**  
Energy is transferred as work is done against the resistance.



Advantages	Disadvantages
<b>Used to heat objects</b>	<b>Efficiency is reduced</b>
Toasters have a coil of wire with high resistance. Current flows and wire glows red giving off IR radiation. IR radiation transfers energy to bread.	Less energy transferred as useful, more 'wasted' as thermal.
Lamps and heaters work in the same way.	Too hot, components may melt and circuit stops working.

## Transferring energy by electricity

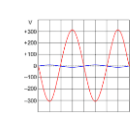


Alternating current	Direct current
<b>p.d. switches direction many times a second, current switches direction</b>	<b>p.d. remains in one direction, current flows the same direction</b>
Generator.	Cell or battery.

Mains supply  
**Frequency 50Hz, 230V**

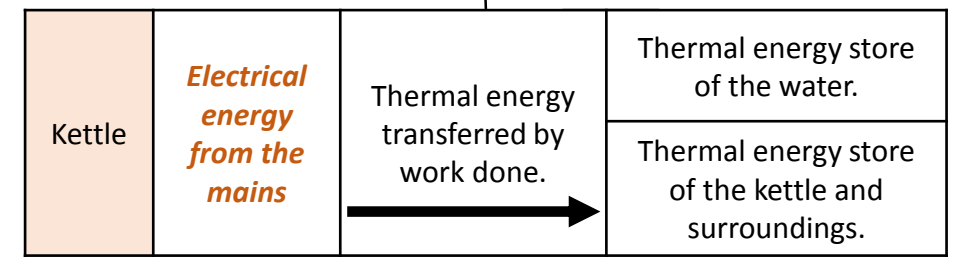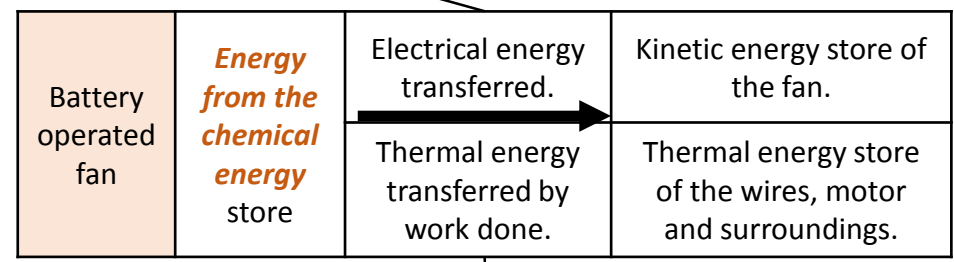

Energy transferred	<b>Joules (J)</b>
Potential difference	<b>Volts (V)</b>
Power	<b>Watts (W)</b>
Current	<b>Amps (A)</b>
Time	<b>Seconds (s)</b>
Resistance	<b>Ohms (Ω)</b>

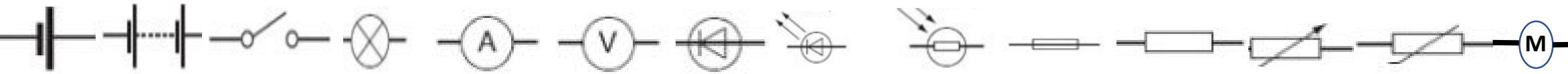

Store of chemical energy	Two or more cells in series	Breaks circuit, turning current off	Lights when current flows	Measures current	Measures potential difference	Current flows one way	Emits light when current flows	Resistance low in bright light	Melts when current is too high	Affects the size of current flowing	Allows current to be varied	Resistance low at high temp	Converts electrical energy into mechanical energy
--------------------------	-----------------------------	-------------------------------------	---------------------------	------------------	-------------------------------	-----------------------	--------------------------------	--------------------------------	--------------------------------	-------------------------------------	-----------------------------	-----------------------------	---

# EDEXCEL TOPIC 10 ELECTRICITY AND CIRCUITS

## Current, Potential difference, Charge and Energy.

## Atom structure

Charge	Size	Found
+	1	In the nucleus
None	1	
-	Tiny	Orbits the nucleus

Set up in series with components	Measures current in amps in the component
Set up parallel to components	Measures p.d. in volts across the component

A circuit with one loop
A circuit with two or more loops

The energy transferred by a component for every per unit of charge passed	1 volt = 1 joule per coulomb (1V = 1J/C)
---	--

$E = Q \times V$  Energy transferred = Charge moved X potential difference

$Q = I \times t$  Charge = Current X time

Current is conserved at a junction in a circuit.

$V = I \times R$  Potential difference = Current X Resistance

Ammeter reading are the same.	Volt meter readings are shared.	Total resistance increases as you add resistors in series.
Ammeters readings are shared between branches.	Volt meter readings are the same.	Total resistance decreases as you add resistors in parallel.

Flow of electrical charge	Ampere (A)
How much electrical work is done by a cell	Volt (V)
Amount of electricity travelling in a circuit	Coulomb (C)

Current in metals is the flow of electrons.


Current only flows when the circuit is closed and there is a p.d. across a component.

### Core Practical

**Relationship between p.d., current and resistance of a lamp and resistor**

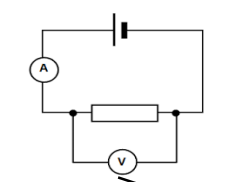**To test series and parallel circuits using resistors and lamps**

Circuit set up like standard test circuit.



**A measurement of how much current flow is reduced**

The higher the resistance, the more difficult it is for current to flow.

Increasing resistance, reduces current.

Increasing voltage, increases current.

Used to investigate relationship between current, p.d. and resistance of components

Insert variable resistor, in series, to change current and measure current and p.d.

Joules (J)
Coulombs (C)
Volts (V)
Amps (A)
Seconds (s)
Ohms (Ω)




Resistance varies with temperature	Resistance varies with light intensity
Resistance decreases as temperature increases.	Resistance decreases as light increases.

At a constant temperature, current is directly proportional to the p.d. across the resistor.

As current increases, the resistance increases. The temperature increases as current flows.

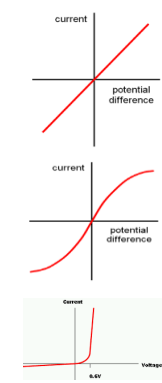Current flows when p.d. flows forward. Very high resistance in reverse.





$$P = E \div t$$

$$\text{Power} = \text{Energy transferred} \div \text{time}$$

<b>Live - Brown</b>	Carries p.d from mains supply.	p.d between live and earth = 230V
<b>Neutral - Blue</b>	Completes the circuit.	p.d. = 0V
<b>Earth - Green and Yellow stripes</b>	Only carries current if there is a fault.	p.d. = 0V

**HIGHER ONLY**

Use low resistance metals in wire. Thicker wires have lower resistance. Resistance can be decreased by cooling wires so the lattice ions do not vibrate as much.

**Electrons flow through lattice of vibrating ions, they collide with ions.** The more collisions, the harder it is for electrons to pass through so higher electrical resistance.

Thermal energy dissipates into surroundings thermal energy store and the temperature rises.

Energy transferred by heating and the resistor becomes warmer.

**When current flows circuits warm up** Energy is transferred as work is done against the resistance.

<b>Used to heat objects</b>	<b>Efficiency is reduced</b>
Toasters have a coil of wire with high resistance. Current flows and wire glows red giving off IR radiation. IR radiation transfers energy to bread.	Less energy transferred as useful, more 'wasted' as thermal.
	Too hot, components may melt and circuit stops working.

Lamps and heaters work in the same way.

<b>Fuse</b>	Thin wire inside the plug connected to live wire.	If current exceeds a certain value, the wire melts breaking the circuit.
<b>Circuit breaker</b>	'Trips' the switch.	Detect change in current and switch off the supply.
<b>Switch</b>	Connected to the live wire.	When turned off, no current goes through the appliance.
<b>Earthing</b>	Earth wire joins the metal case.	Earth wire takes current to the ground instead of conducting in the metal.


**Electrical safety**

**A connection between the live wire and earth** The live wire carries 230V, your body is at 0V so there is a large potential difference across your body and current flows through you.

**Power rating measured in watts** The power rating equals the number of joules transferred every second by the device from mans electrical supply to an energy store.

**EDEXCEL TOPIC 10 ELECTRCITY AND CIRCUITS**

**Transferring energy**

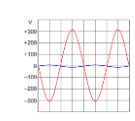

<b>p.d. switches direction many times a second, current switches direction</b>	<b>p.d. remains in one direction, current flows the same direction</b>
Generator.	Cell or battery.

**Frequency 50Hz, 230V**

**Power**

**Energy transferred per second** Measured in Watts (W).

**Depends on p.d. across and current flowing through device** Current equals how much charge passes per unit time. p.d. equals how much energy each unit of charge transfers. Both affect the rate of energy transfer and the rate at which energy is transferred to other energy stores.

Power (W) = current X potential difference  $P = I \times V$


Power = (current)<sup>2</sup> X resistance  $P = I^2 \times R$

**Transferring energy by electricity**

<b>Energy from the chemical energy store</b>	Electrical energy transferred.	Kinetic energy store of the fan.
	Thermal energy transferred by work done.	Thermal energy store of the wires, motor and surroundings.

<b>Electrical energy from the mains</b>	Thermal energy transferred by work done.	Thermal energy store of the water.
		Thermal energy store of the kettle and surroundings.

	<b>Joules (J)</b>
	<b>Volts (V)</b>
	<b>Watts (W)</b>
	<b>Amps (A)</b>
	<b>Seconds (s)</b>
	<b>Ohms (Ω)</b>

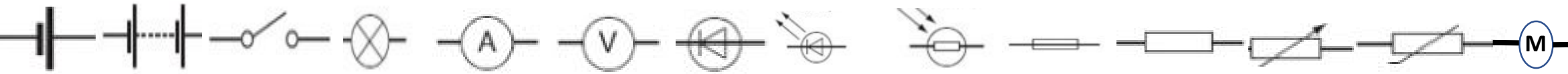

Cell	Battery	Switch	Lamp	Ammeter	Volt meter	Diode	LED	LDR	Fuse	Resistor	Variable resistor	Thermistor	Motor

# EDEXCEL TOPIC 10 ELECTRICITY AND CIRCUITS

## Current, Potential difference, Charge and Energy.

## Atom structure

## Electric Circuits

## Resistance

Particle			
Proton			
Neutron			
Electron			

Ammeter	Measures current in amps in the component
Volt meter	Measures p.d. in volts across the component

Series	
Parallel	

Potential difference	1 volt = 1 joule per coulomb (1V = 1J/C)
----------------------	--

$E = Q \times V$  Energy transferred = Charge moved X potential difference

$Q = I \times t$  Charge = Current X time

Current is conserved at a junction in a circuit.

$V = I \times R$  Potential difference = Current X Resistance

Current	Ampere (A)
Potential difference (p.d.)	Volt (V)
Charge	Coulomb (C)

Current in metals is the flow of electrons.

Current only flows when the circuit is closed and there is a p.d. across a component.

### Core Practical

Circuit set up like standard test circuit.

### Standard test circuit

Resistance Ohms ( $\Omega$ )

The higher the resistance, the more difficult it is for current to flow.

Increasing resistance, reduces current.

Increasing voltage, increases current.


Insert variable resistor, in series, to change current and measure current and p.d.

Energy transferred	
Charge	
Potential difference	
Current	
Time	
Resistance	



Thermistor	LDR
Resistance decreases as temperature increases.	Resistance decreases as light increases.

Fixed resistor	
Filament lamp	
Diode	

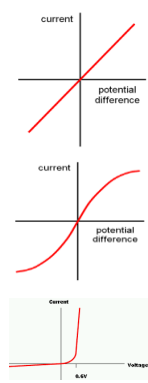

# EDEXCEL TOPIC 10 ELECTRICITY AND CIRCUITS

3 pin plug	Carries p.d from mains supply.	p.d between live and earth = 230V
	Completes the circuit.	p.d. = 0V
	Only carries current if there is a fault.	p.d. = 0V

**HIGHER ONLY**

**Reducing unwanted energy transfer**  
Use low resistance metals in wire. Thicker wires have lower resistance. Resistance can be decreased by cooling wires so the lattice ions do not vibrate as much.

$$P = E \div t$$

Power = Energy transferred ÷ time

**Energy transfer**  
The more collisions, the harder it is for electrons to pass through so higher electrical resistance.

Thermal energy dissipates into surroundings thermal energy store and the temperature rises.


Energy transferred by heating and the resistor becomes warmer.

**Current in a resistor**  
Energy is transferred as work is done against the resistance.

Advantages	Disadvantages
Toasters have a coil of wire with high resistance. Current flows and wire glows red giving off IR radiation. IR radiation transfers energy to bread.	Less energy transferred as useful, more 'wasted' as thermal. Too hot, components may melt and circuit stops working.

Lamps and heaters work in the same way.

## Transferring energy

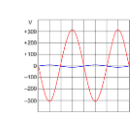

Alternating current	Direct current
Generator.	Cell or battery.

Mains supply

## Power

**Power**  
Measured in Watts (W).

**Power transfer**  
Both affect the rate of energy transfer and the rate at which energy is transferred to other energy stores.

Current equals how much charge passes per unit time.

p.d. equals how much energy each unit of charge transfers.

$$Power (W) = current \times potential\ difference \quad P = I \times V$$


$$Power = (current)^2 \times resistance \quad P = I^2 \times R$$

## Transferring energy by electricity

**Battery operated fan**  
Electrical energy transferred. → Kinetic energy store of the fan.  
Thermal energy transferred by work done. Thermal energy store of the wires, motor and surroundings.

**Kettle**  
Thermal energy transferred by work done. → Thermal energy store of the water.  
Thermal energy store of the kettle and surroundings.

Energy transferred	
Potential difference	
Power	
Current	
Time	
Resistance	

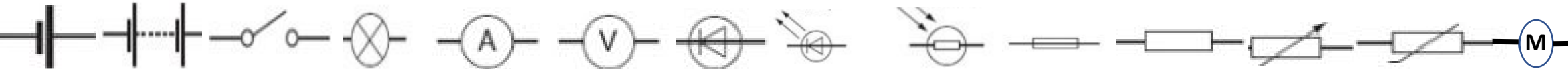

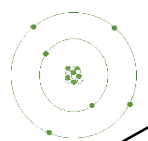
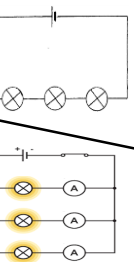

Electric Circuits

Atom structure

Current, Potential difference, Charge and Energy.

EDEXCEL TOPIC 10 ELECTRICITY AND CIRCUITS

Resistance



$E = Q \times V$

$Q = I \times t$


Current is


$V = I \times R$


Current in

Current only


Core Practical	

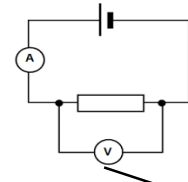

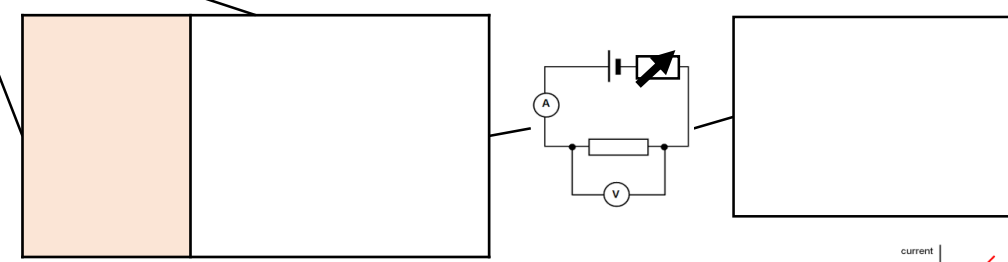

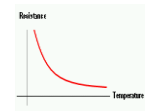

**EDEXCEL  
TOPIC 10  
ELECTRICITY AND  
CIRCUITS**

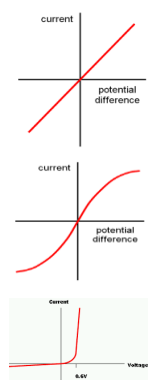**Electrical  
safety**

**Transferring energy**

**Transferring  
energy by  
electricity**

**Power**

HIGHER ONLY


Current in a resistor

*When current flows circuits warm up*

Energy is transferred as work is done against the resistance.

Thermal energy

Energy

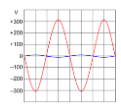

Current

p.d.

$P = I \times V$

$P = I^2 \times R$

