

# Computational Logic

## AND



Both inputs must be positive to get a positive result

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

## OR



At least one input must be positive to get a positive result


A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

## NOT



The output is the opposite of the input

A	Z
0	1
1	0

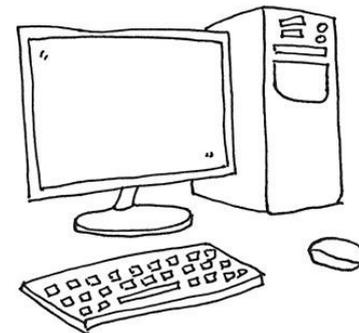


## TRUTH TABLES

Create a column for each input needed and use binary counting to populate it with data (i.e. if there are 4 inputs you need 4 input columns). In this example we will use binary counting with 4 bits to fill the table, 0000, 0001, 0010, 0011 etc. Create a column for each output (i.e. if there are 4 logic gates used, there will be 4 outputs) and label each input and output column with a different letter of the alphabet.

Work out each output column using the correct input columns, in this example W (an OR gate) would only be using inputs A and B. Continue until all columns have been populated.

## COMBINING LOGIC GATES

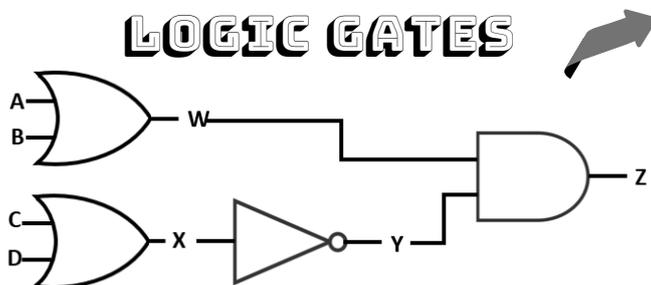

## Shorthand

When writing logic problems, shorthand is often used to represent AND, OR and NOT.

$$A \text{ AND } B = A \wedge B$$

$$A \text{ OR } B = A \vee B$$

$$\text{NOT } A = \neg A$$

## Computing-related Mathematics

Addition + (3 + 4 = 7)

Subtraction - (12 - 3 = 9)

Multiplication \* (3 \* 4 = 13)

Division / (100 / 4 = 25)

Exponentiation (to the power of) ^ (10 ^ 3 = 1000)

Whole number division DIV (13 DIV 5 = 2)


Remainder after whole number division MOD (13 MOD 5 = 3)



Inputs				Outputs			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	0
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	0
0	0	1	1	0	1	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	1	0	0
0	1	1	0	1	1	0	0
0	1	1	1	1	1	0	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	0
1	1	0	0	1	0	1	1
1	1	0	1	1	1	0	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	0	0



(C) Nichola Wilkin Ltd 2019

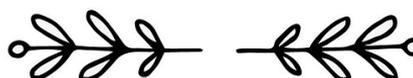

# Computational Logic

## Revise it

Read through the handout and then select a revision technique from those described in this section, you can even do more than one if you want!

### Highlight

Highlight key words (maximum of 2 per sentence) and then cover the page and try to write down all the key words you can remember. Go back and fill in all the ones you have missed.

### Mind map

Using the handout, draw a mind map and include as many colours, images and diagrams as you can to illustrate it



### BULLET POINTS

Write the main headings (leaving space between each) and then write bullet points of the main key points you need to remember under each heading. Re-read the handout and add any missed points to your list.

### Post-it notes

Write a key word and the definition on a post-it note and stick them around your study area as a reminder of the terminology.

### Record your notes

Re-write the handout in your own words and record yourself using your phone as you read your notes aloud.

## TEST YOURSELF

Cover your notes and the answer before you attempt to answer this practice exam question.


Draw the logic circuit and a truth table for  $(\neg A) \vee (B \wedge C)$  [8 marks]

### Mark your answer

Give a maximum of three points for the logic circuit and a maximum of 5 points for the truth table using the points below as a guide
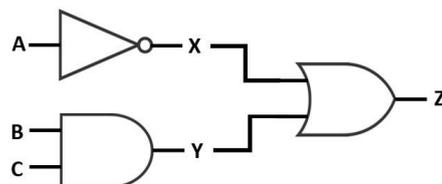
#### Logic circuit:

- Input a going into a NOT gate
- Inputs B and C going into an AND gate
- The output of the two other gates going into an OR gate



#### Truth table:

- Three input columns created and correctly labelled
- Input data filled in (ideally using binary counting)
- An output column showing correct data for NOT A
- An output column showing correct data for B AND C
- And output column showing the final results of the two output columns using OR logic.

A	B	C	X (NOT A)	Y (B AND C)	Z (X OR Y)
0	0	0	1	0	1
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	1	1